

**CS9390\_B**

**THE UNIVERSITY OF WARWICK**

**Examination: Summer 2022**

**Paper Code: CS9390\_B**

**Quantum Computing**

---

**Time allowed: 3 hours.**

Exam type: Standard Examination.

Answer **BOTH** questions from Section A and **ONE** question from Section B.

Read carefully the instructions on the answer book.

Calculators are not allowed.

---

---

---

**Section A**      Answer **BOTH** questions.

---


1. (a) Describe the difference between an *entangled* and a *separable* state. [2]
  - (b) You are given a qubit in state  $|\psi\rangle = \alpha_1 |0\rangle + \beta_1 |1\rangle$ , and another qubit in state  $|\phi\rangle = \alpha_2 |0\rangle + \beta_2 |1\rangle$ . Express the joint state of both qubits in the computational basis. [3]
  - (c) Describe the difference between an *pure* and a *mixed* state. Explain how to express a mixed state as a *density matrix*, and describe the three conditions a density matrix must satisfy. [5]
  - (d) For each of the following states, write whether the state is entangled or separable. Then write the mixed state obtained by discarding the second qubit (either as a distribution or as a density matrix). Justify your answers in each case. [20]
    - i.  $\frac{|00\rangle + |11\rangle}{\sqrt{2}}$ .
    - ii.  $\frac{|00\rangle + |01\rangle}{\sqrt{2}}$ .
    - iii.  $\frac{1}{2}(|00\rangle + |01\rangle + |10\rangle + |11\rangle)$ .
    - iv.  $\frac{1}{2}(|00\rangle + |01\rangle + |10\rangle - |11\rangle)$ .
    - v.  $\frac{1}{2}(|00\rangle + i|01\rangle + i|10\rangle - |11\rangle)$ .
-

2. In this question you will show how to attack Wiesner's quantum money scheme if the bank always returns banknotes to the client (even when the verification fails).

(a) Describe how an  $n$ -qubit banknote is generated and verified in Wiesner's quantum money scheme. [8]

(b) Design a quantum circuit which, on input the state  $|0\rangle^{\otimes 3}$ , outputs a random 1-qubit banknote  $|\$_k\rangle$  along with its corresponding key  $k$ . Explain why your circuit works. (Note: your circuit can output any representation of  $k$ .)

Hint: use the controlled- $H$  gate,  $C_H(|b\rangle \otimes |\psi\rangle) = |b\rangle \otimes H^b |\psi\rangle$ , written

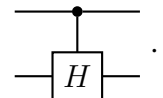

[7]

(c) Suppose you are given a 1-qubit banknote  $|\$_k\rangle$ . You apply an  $X$  gate to  $|\$_k\rangle$ , obtaining a state  $|\phi\rangle$ , and then you send  $|\phi\rangle$  to the bank. The bank runs the verification procedure on  $|\phi\rangle$  and sends you the outcome (VALID or INVALID) along with the post-measurement state. Describe what happens for each possible  $k$ . [8]

(d) Describe how to recover the key  $k$  from an  $n$ -qubit banknote  $|\$_k\rangle$ . [7]

---

**Section B**      Answer **ONE** question.

---


3. For a function  $f: \{0, 1\}^n \rightarrow \{0, 1\}^n$ , denote by  $U_f$  the unitary  $|x, y\rangle \mapsto |x, (y \oplus f(x))\rangle$ .
- (a) Suppose  $n = 1$ . Show how to build a circuit that computes the unitary  $|x\rangle \mapsto (-1)^{f(x)} |x\rangle$  (known as the phase oracle). You may use  $Z$  gates, ancilla qubits initialized to  $|0\rangle$ , and **two**  $U_f$  gates. You must ensure that any ancilla qubits return to the state  $|0\rangle$  so that they can be safely discarded. Prove that your circuit is correct. [6]
- (b) Suppose now (and for the remaining parts of this question) that  $n = 2$ . The gate  $S$  maps  $|0\rangle \mapsto |0\rangle$  and  $|1\rangle \mapsto i|1\rangle$ . Show that  $S^2 = Z$ . [2]
- (c) Show how to build a circuit that computes the unitary that maps  $|x\rangle \mapsto \omega^{2f(x)_1 + f(x)_2} |x\rangle$ , where  $f(x)_1, f(x)_2$  are the first and second bits of  $f(x)$ , respectively. You may use  $S$  gates, ancilla qubits initialised to  $|0\rangle$ , and **two**  $U_f$  gates. You must ensure that any ancilla qubits return to the state  $|0\rangle$  so that they can be safely discarded. Prove that your circuit is correct. [12]
- (d) Design a circuit that determines whether  $f$  is constant or one-to-one. You may use:
- any number of qubits initialized to  $|0\rangle$ ,
  - Hadamard ( $H$ ) gates,
  - $S$  gates,
  - measurements in the computational basis, and
  - **two**  $U_f$  gates.
- Prove that your circuit is correct. [20]
-

4. (a) Describe the CNOT and Toffoli (CCNOT) gates. [6]

(b) What are the eigenvectors and eigenvalues of the matrix  $X = \begin{pmatrix} 0 & 1 \\ 1 & 0 \end{pmatrix}$ ? [4]

(c) Using your answer to the above, or otherwise, find a matrix  $\sqrt{X}$  such that  $(\sqrt{X})^2 = X$ . (Hint: observe that  $X$  is Hermitian.) [6]

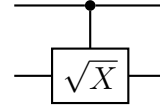(d) The controlled- $\sqrt{X}$  gate  $C_{\sqrt{X}}$  is drawn like this:



and operates as follows:

$$C_{\sqrt{X}} |0\rangle \otimes |\psi\rangle = |0\rangle \otimes |\psi\rangle \quad C_{\sqrt{X}} |1\rangle \otimes |\psi\rangle = |1\rangle \otimes \sqrt{X} |\psi\rangle$$

for any qubit state  $|\psi\rangle$ .

i. Show how to implement a CNOT gate using only  $C_{\sqrt{X}}$  gates. [4]

ii. Show how to implement the gate  $(C_{\sqrt{X}})^\dagger$  using only  $C_{\sqrt{X}}$  gates. [4]

iii. Show how to implement the unitary  $U$  that maps

$$|ab\rangle \otimes |\psi\rangle \mapsto |ab\rangle \otimes (\sqrt{X})^a (\sqrt{X})^b |\psi\rangle$$

for all  $a, b \in \{0, 1\}$  and qubit states  $|\psi\rangle$  using only  $C_{\sqrt{X}}$  gates. [6]

iv. Show how to implement a Toffoli gate using only  $C_{\sqrt{X}}$ ,  $(C_{\sqrt{X}})^\dagger$  and CNOT gates. (Hint: start with your circuit from part (iii).) [10]

(In each part, you should draw a circuit and show that it is correct.)